


SAINIK SCHOOL GOPALGANJ

CLASS-XII


Chapter Current Electricity

Assignment

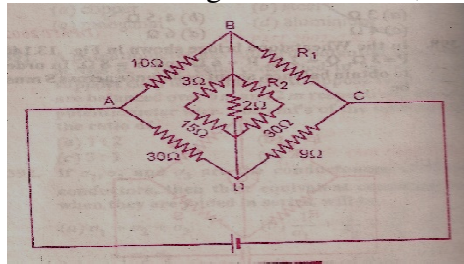
- Q.1 n cells each of emf E and internal resistance r send the same current through an external resistance R whether the cells are connected in series or in parallel. Then
 (a) $R = nr$ (b) $R = r$ (c) $r = nR$ (d) $R = \sqrt{nr}$ (e) $r = \sqrt{nR}$
- Q.2 In a Meter-bridge with a standard resistance of 5Ω in the left gap, the ratio of balancing lengths on the Meter bridge wire is $2 : 3$. The unknown resistance is
 (a) 1Ω (b) 15Ω (c) 10Ω (d) 3.3Ω (e) 7.5Ω
- Q.3 In the Wheatstone bridge shown below, in order to balance the bridge, we must have



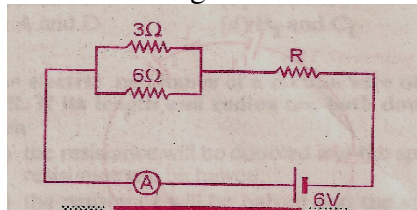- (a) $R_1 = 3 \Omega ; R_2 = 3 \Omega$ (b) $R_1 = 6 \Omega ; R_2 = 15 \Omega$
 (c) $R_1 = 1.5 \Omega ; R_2 = \text{any finite value}$ (d) $R_1 = 3 \Omega ; R_2 = \text{any finite value}$
 (e) $R_2 = 1.5 \Omega ; R_1 = \text{any finite value}$
- Q.4 In a Wheatstone bridge all the four arms have equal resistance R . If the resistance of the galvanometer arm is also R , the equivalent resistance of the combination as seen by the battery is
 (a) $\frac{R}{4}$ (b) $\frac{R}{2}$ (c) R (d) $2R$
- Q.5 The current in a conductor varies with time t as $I = 2t + 3t^2$ where I is in ampere and t in seconds. Electric charge flowing through a section of the conductor during $t = 2$ sec to $t = 3$ sec is
 (a) 10 C (b) 24 C (c) 33 C (d) 44 C
- Q.6 If the ammeter in the given circuit reads 2A , the resistance R is




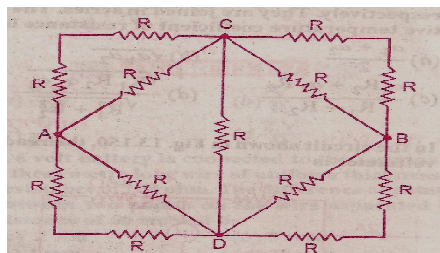- (a) 1Ω (b) 2Ω (c) 3Ω (d) 4Ω
- Q.7 Thirteen resistance each of resistance $R \Omega$ are connected in the circuit as shown in the Fig . The effective resistance between A and B is



- (a) $2R \Omega$ (b) $4R/3 \Omega$ (c) $2R/3 \Omega$ (d) $R \Omega$

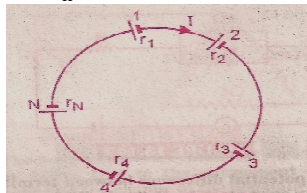
- Q.8 A group of N cells where e.m.f. varies directly with the internal resistance as per the equation $E_N = 1.5 r_n$ are connected as shown in the Fig. The current I in the circuit is



- (a) 0.51 A (b) 5.1 A (c) 0.15 A (d) 1.5 A
- Q.9 Two wires of resistances R_1 and R_2 have temperature coefficient of resistance α_1 and α_2 respectively. They are joined in series. The effective temperature coefficient of resistance is

- (a) $\frac{\alpha_1 + \alpha_2}{2}$ (b) $\sqrt{\alpha_1 \alpha_2}$ (c) $\frac{\alpha_1 R_1 + \alpha_2 R_2}{R_1 + R_2}$ (d) $\frac{\sqrt{R_1 R_2 + \alpha_1 \alpha_2}}{\sqrt{R_1^2 + R_2^2}}$

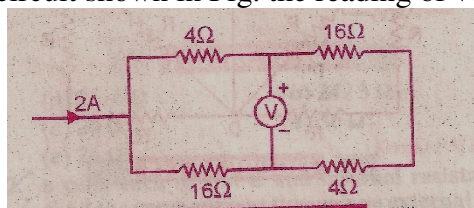- Q.10 In the circuit shown in Fig. the reading of voltmeter is



- (a) 12 V (b) 8 V (c) 20 V (d) 16 V
- Q.11 A cell of Internal resistance 2Ω and e.m.f. 10 volt is connected to a uniform wire of length 500 cm and resistance 3Ω . The potential gradient in the wire is.


- (a) 30 mV/cm (b) 12 mV/cm (c) 20 m V/cm (d) 4 mV/cm
- Q.12 Which of the following has negative temperature coefficient of resistance ?
- (a) copper (b) aluminium (c) iron (d) germanium

- Q.13 The resistance of the series combination of two resistance is S . When they are joined in parallel the total resistance is P . If $S = n P$, then the minimum possible value of n is

- (a) 4 (b) 3 (c) 2 (d) 1
- Q.14 An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If lengths and radii of the wires are in the ratio of $4/3$ and $2/3$, then the ratio of the currents passing through the wires will be

- (a) 3 (b) $1/3$ (c) $8/9$ (d) 2
- Q.15 In a metre bridge experiment null point is obtained at 20 cm from one end of the wire when resistance X is balanced against another resistance Y . If $X < Y$, then where will be new position of the null point from the same end, if one decides to balance a resistance of $4 X$ against Y

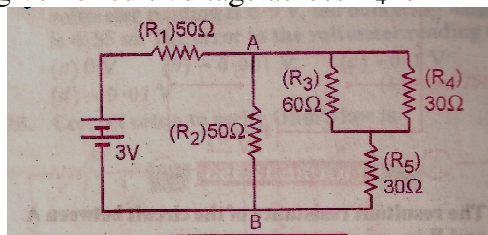- (a) 50 cm (b) 80 cm (c) 40 cm (d) 70 cm
- Q.16 In the given circuit voltage across R_4 is



- (a) 0.4 V (b) 0.6 V (c) 0.8 V (d) 1.0 V
- (e) 1.2 V
- Q.17 When a body is earth connected, electrons from the earth flow into the body. This means the body is

- (a) charged negatively (b) an insulator (c) unchanged
 (d) charged positively

Q.18 A cube is constructed from 12 identical wires. Current enters one corner of the cube and it leaves the opposite corner. If the resistance of each wire is r , then equivalent resistance will be

- (a) $6r/5$ (b) $5r/6$ (c) $5r/12$ (d) $12r/5$


Q.19 A source of e.m.f. $E = 15\text{ V}$ and having negligible internal resistance is connected to a variable resistance, so that the current in the circuit increases with time as $I = 1.2t + 3$. Then the total charge that will flow in first five second will be

- (a) 10 C (b) 20 C (c) 30 C (d) 40 C

Q.20 When a wire of uniform cross-section a , length l and resistance R is bent into a complete circle, resistance between any two of diametrically opposite points will be :

- (a) $\frac{R}{2}$ (b) $\frac{R}{4}$ (c) $\frac{R}{8}$ (d) $4R$

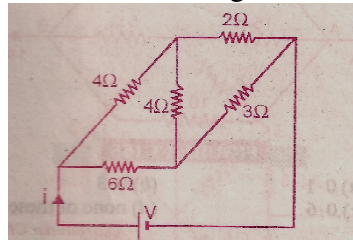Q.21 For the network shown in the Fig. the value of the current I is :



- (a) $\frac{18\text{ V}}{5}$ (b) $\frac{5\text{ V}}{9}$ (c) $\frac{9\text{ V}}{35}$ (d) $\frac{5\text{ V}}{18}$

Q.22 Two sources of equal emf are connected to an external resistance R . The internal resistances of the two sources are R_1 and R_2 ($R_2 > R_1$). If the potential difference across the source having internal resistance R_2 is zero, then.

- (a) $R = R_1 R_2 / (R_2 - R_1)$ (b) $R = R_1 R_2 / (R_1 + R_2)$
 (c) $R = R_2 - R_1$ (d) $R = R_2 \times (R_1 + R_2) / (R_2 - R_1)$

Q.23 In a potentiometer experiment, the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of 2Ω , the balancing length becomes 120 cm. The internal resistance of the cell is

- (a) 2Ω (b) 4Ω (c) 0.5Ω (d) 1Ω

Q.24 To draw the maximum current from a combination of cells, how should the cells be grouped ?

- (a) series (b) parallel (c) mixed
 (d) depends upon the relative values of external and internal resistance

Q.25 A wire is cut into 4 pieces, which are put together by sides to obtain one conductor. If the original resistance of wire was R , the resistance of the bundle will be

- (a) $R/4$ (b) $R/8$ (c) $R/16$ (d) $R/32$