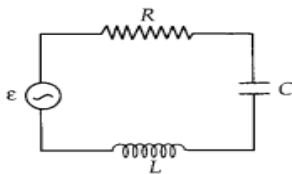


SAINIK SCHOOL GOPALGANJ
CLASS – XII
ASSIGNMENT – ALTERNATING CURRENT

1. A $100\ \Omega$ resistor is connected to a $220\ \text{V}$, $50\ \text{Hz}$ ac supply.
 - (a) What is the rms value of current in the circuit?
 - (b) What is the net power consumed over a full cycle?
2.
 - (a) The peak voltage of an ac supply is $300\ \text{V}$. What is the rms voltage?
 - (b) The rms value of current in an ac circuit is $10\ \text{A}$. What is the peak current?
3. A $44\ \text{mH}$ inductor is connected to $220\ \text{V}$, $50\ \text{Hz}$ ac supply. Determine the rms value of the current in the circuit.
4. A $60\ \mu\text{F}$ capacitor is connected to a $110\ \text{V}$, $60\ \text{Hz}$ ac supply. Determine the rms value of the current in the circuit.
5. In question no. 3 and 4, what is the net power absorbed by each circuit over a complete cycle. Explain your answer.
6. Obtain the resonant frequency ω_0 of a series LCR circuit with $L = 2.0\ \text{H}$, $C = 32\ \mu\text{F}$ and $R = 10\ \Omega$. What is the Q -value of this circuit?
7. A charged $30\ \mu\text{F}$ capacitor is connected to a $27\ \text{mH}$ inductor. What is the angular frequency of free oscillations of the circuit?
8. Suppose the initial charge on the capacitor in question 7 is $6\ \text{mC}$. What is the total energy stored in the circuit initially? What is the total energy at later time?
9. A series LCR circuit with $R = 20\ \Omega$, $L = 1.5\ \text{H}$ and $C = 35\ \mu\text{F}$ is connected to a variable-frequency $200\ \text{V}$ ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?
10. A radio can tune over the frequency range of a portion of MW broadcast band: ($800\ \text{kHz}$ to $1200\ \text{kHz}$). If its LC circuit has an effective inductance of $200\ \mu\text{H}$, what must be the range of its variable capacitor?
11. Figure (i) shows a series LCR circuit connected to a variable frequency $230\ \text{V}$ source. $L = 5.0\ \text{H}$, $C = 80\ \mu\text{F}$, $R = 40\ \Omega$.



Fig(i)

- (a) Determine the source frequency which drives the circuit in resonance.
- (b) Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- (c) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.
12. Show that in the free oscillations of an LC circuit, the sum of energies stored in the capacitor and the inductor is constant in time.
13. A sinusoidal voltage of peak value 283 V and frequency 50 Hz is applied to a series LCR circuit in which $R = 3 \Omega$, $L = 25.48 \text{ mH}$, and $C = 796 \mu\text{F}$. Find
- (a) the impedance of the circuit;
- (b) the phase difference between the voltage across the source and the current;
- (c) the power dissipated in the circuit; and
- (d) the power factor.
14. (a) For circuits used for transporting electric power, a low power factor implies large power loss in transmission. Explain.
- (b) Power factor can often be improved by the use of a capacitor of appropriate capacitance in the circuit. Explain.
15. A resistor of 200Ω and a capacitor of $15.0 \mu\text{F}$ are connected in series to a 220 V, 50 Hz ac source.
- (a) Calculate the current in the circuit;
- (b) Calculate the voltage (rms) across the resistor and the capacitor. Is the algebraic sum of these voltages more than the source voltage? If yes, resolve the paradox.